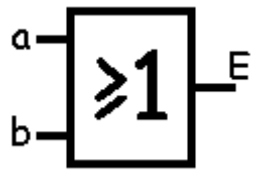
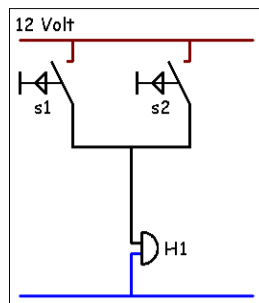
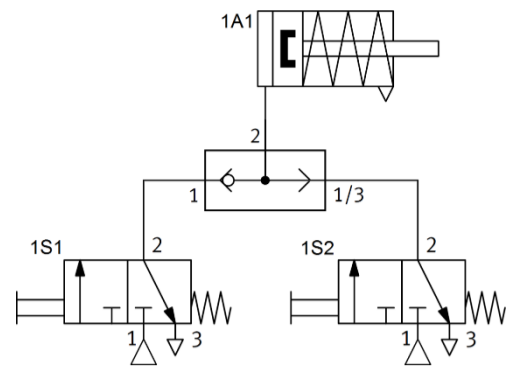
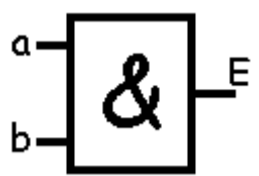
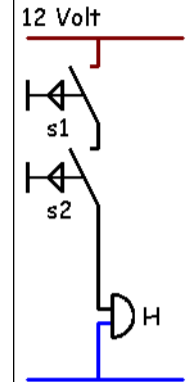
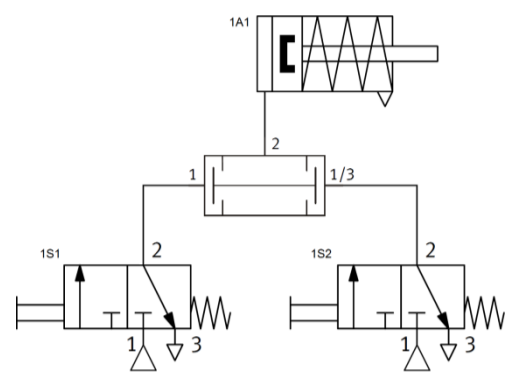
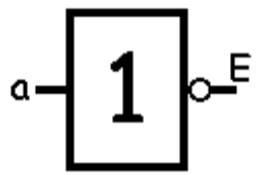
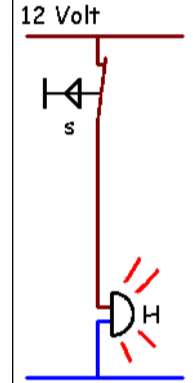
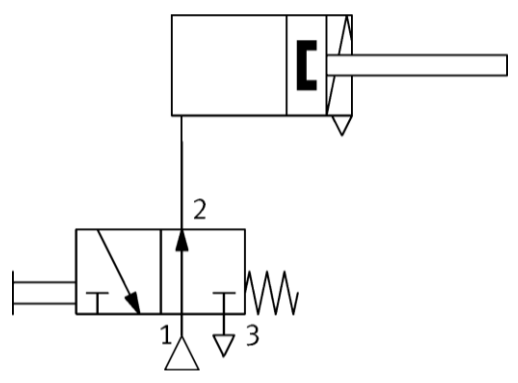
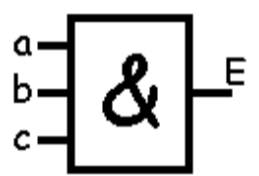
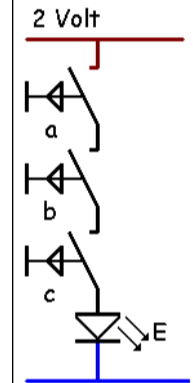
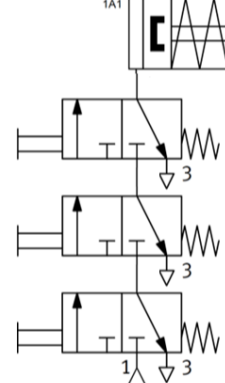
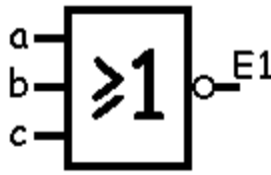
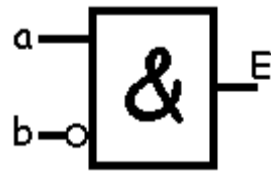
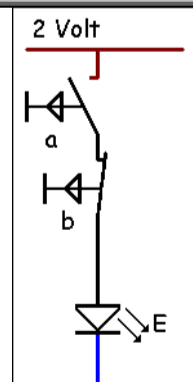
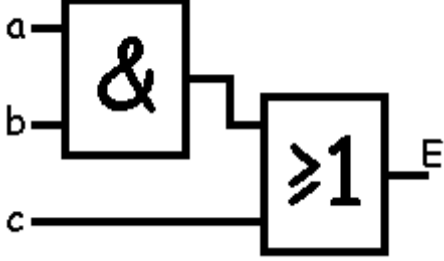
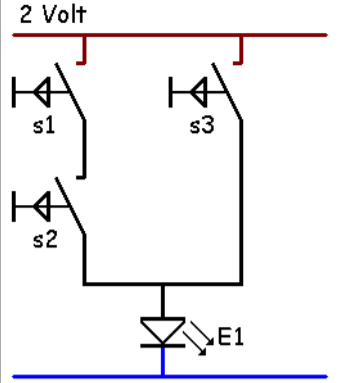
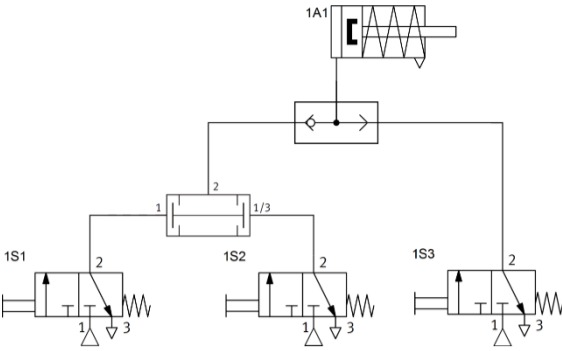
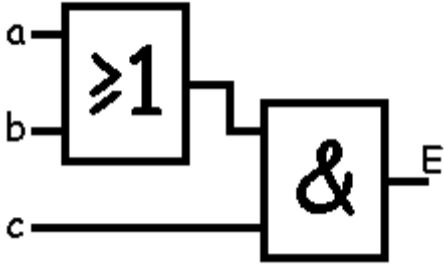
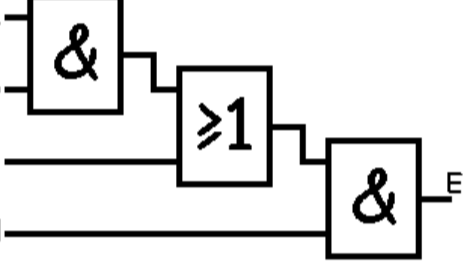


Aanduiding	Functie/Schakeling	Waarheidstabel	Elektrisch	Pneumatisch																																				
OF / OR	 Formule $E = a + b$	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>E</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	E	0	0	0	1	0	1	0	1	1	1	1	1																							
a	b	E																																						
0	0	0																																						
1	0	1																																						
0	1	1																																						
1	1	1																																						
EN / AND	 Formule $E = a \cdot b$	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>E</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	E	0	0	0	1	0	0	0	1	0	1	1	1																							
a	b	E																																						
0	0	0																																						
1	0	0																																						
0	1	0																																						
1	1	1																																						
Niet / NOT	 Formule $E = \bar{a}$	<table border="1"> <thead> <tr> <th>a</th> <th>E</th> </tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	a	E	0	1	1	0																																
a	E																																							
0	1																																							
1	0																																							
EN / AND	 Formule $E = a \cdot b \cdot c$	<table border="1"> <thead> <tr> <th>a</th> <th>B</th> <th>C</th> <th>E</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	B	C	E	0	0	0	0	1	0	0	0	0	1	0	0	1	1	0	0	0	0	1	0	1	0	1	0	0	1	1	0	1	1	1	1		
a	B	C	E																																					
0	0	0	0																																					
1	0	0	0																																					
0	1	0	0																																					
1	1	0	0																																					
0	0	1	0																																					
1	0	1	0																																					
0	1	1	0																																					
1	1	1	1																																					
NOF / NOR	 Formule $E = \overline{a + b + c}$	<table border="1"> <thead> <tr> <th>a</th> <th>B</th> <th>c</th> <th>E1</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	a	B	c	E1	0	0	0	1	1	0	0	0	0	1	0	0	1	1	0	0	0	0	1	0	1	0	1	0	0	1	1	0	1	1	1	0		
a	B	c	E1																																					
0	0	0	1																																					
1	0	0	0																																					
0	1	0	0																																					
1	1	0	0																																					
0	0	1	0																																					
1	0	1	0																																					
0	1	1	0																																					
1	1	1	0																																					
EN / AND	 Formule $E = a \cdot \bar{b}$	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>E</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	a	b	E	0	0	0	1	0	1	0	1	0	1	1	0																							
a	b	E																																						
0	0	0																																						
1	0	1																																						
0	1	0																																						
1	1	0																																						

Aanduiding	Functie/Schakeling	Waarheidstabel	Elektrisch	Pneumatisch																																																																																					
En / OF	 <p>Formule $E = a \cdot b + c$</p>	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>c</th> <th>E</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	c	E	0	0	0	0	1	0	0	0	0	1	0	0	1	1	0	1	0	0	1	1	1	0	1	1	0	1	1	1	1	1	1	1																																																			
a	b	c	E																																																																																						
0	0	0	0																																																																																						
1	0	0	0																																																																																						
0	1	0	0																																																																																						
1	1	0	1																																																																																						
0	0	1	1																																																																																						
1	0	1	1																																																																																						
0	1	1	1																																																																																						
1	1	1	1																																																																																						
OF / EN	 <p>Formule $E = a + b \cdot c$</p>	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>c</th> <th>E</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	c	E	0	0	0	0	1	0	0	0	0	1	0	0	1	1	0	0	0	0	1	0	1	0	1	1	0	1	1	1	1	1	1	1																																																			
a	b	c	E																																																																																						
0	0	0	0																																																																																						
1	0	0	0																																																																																						
0	1	0	0																																																																																						
1	1	0	0																																																																																						
0	0	1	0																																																																																						
1	0	1	1																																																																																						
0	1	1	1																																																																																						
1	1	1	1																																																																																						
EN / OF / EN	 <p>Formule $E = (a \cdot b + c) \cdot d$</p>	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>c</th> <th>d</th> <th>E</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	c	d	E	0	0	0	0	0	1	0	0	0	0	0	1	0	0	0	1	1	0	0	0	0	0	1	0	0	1	0	1	0	0	0	1	1	0	0	1	1	1	0	0	0	0	0	1	0	1	0	0	1	0	0	1	0	1	0	1	1	0	1	1	0	0	1	1	1	1	0	1	1	1	0	1	1	1	1	1	1	1	1	1		
a	b	c	d	E																																																																																					
0	0	0	0	0																																																																																					
1	0	0	0	0																																																																																					
0	1	0	0	0																																																																																					
1	1	0	0	0																																																																																					
0	0	1	0	0																																																																																					
1	0	1	0	0																																																																																					
0	1	1	0	0																																																																																					
1	1	1	0	0																																																																																					
0	0	0	1	0																																																																																					
1	0	0	1	0																																																																																					
0	1	0	1	0																																																																																					
1	1	0	1	1																																																																																					
0	0	1	1	1																																																																																					
1	0	1	1	1																																																																																					
0	1	1	1	1																																																																																					
1	1	1	1	1																																																																																					